

KJ-1378

B.Sc. (Part - III)

Term End Examination, 2020

INFORMATION TECHNOLOGY

Paper - I

Amplifiers and Oscillators

Time: Three Hours] [Maximum Marks: 50]

Note: Answer any **two** parts from each question. All questions carry equal marks.

Unit-I

- **1.** (a) Explain power amplifier and its types.
 - (b) Explain the advantages and distortions of pushpull power amplifier.
 - (c) Distinguish between power dissipation curve and harmonic dissipation curve.

290_JDB_*_(3)

(Turn Over)

Unit-II

- **2.** (a) Explain feedback amplifier and its types.
 - (b) Derive the input and output impedence in voltage series feedback.
 - (c) Explain oscillator and Barkhausen criteria.

Unit-III

- **3.** (a) Differentiate between Differential amplifier and Operational amplifier.
 - (b) Write short notes on the following:
 - (i) Current driff
 - (ii) Input bias current
 - (c) Explain how an Op-Amp can be used as differentiator.

Unit-IV

- **4.** (a) Draw the pin diagram of 8085 microprocessor.
 - (b) Explain different I/O and machine controlled instructions.
 - (c) Explain different addressing modes with example.

Unit-V

5. (a) Explain machine language and assembly languages in detail.

290_JDB_*_(3)

(Continued)

(b) Explain the data transfer operations and its instruction set with example.

(c) Write an Assembly language program of 8085 to add 100 integer numbers.

290_JDB_★_(3)